

# LAB REPORT No. 04:

## REGISTERS

---



By:

Jiaqing Wan(16), Jiaxin Zheng(19)

Instructor: Dr. Xi Zhou

Classnumber: ZM1501

NAU ID:

5358836, 5358840

October 22, 2017

## I. INTRODUCTION

### A. Objectives

At the completion of this lab, the student will be able to:

1. Complete a VHDL design from a functional specification (write VHDL, simulate functional behavior, and demonstrate functional behavior on the Cyclone V demo board) for sequential circuits.

### B. Background knowledge

The Accumulator is a register that stores results from the ALU and later feeds those results back into the ALU for more processing. Its connection to the ALU is:

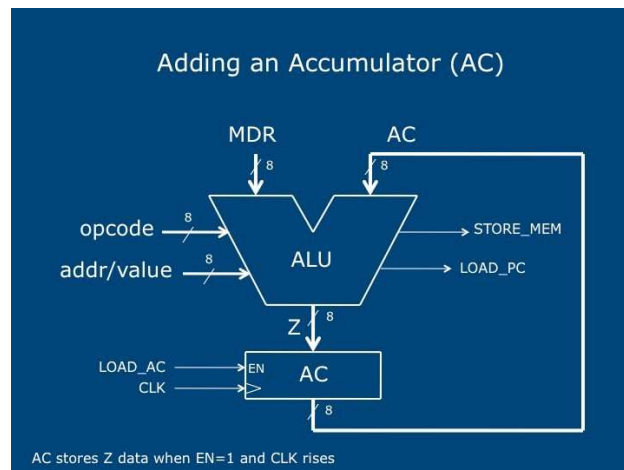


FIG. I.1 Accumulator in ALU

The Instruction Register holds the instruction that was most recently fetched from memory. As described below, the instruction field is two bytes (16 bits) wide, with the upper byte being the opcode and the lower byte being the address or value information. Since our data bus is only 8 bits wide, we will usually fetch instructions in two different memory read operations. The first read cycle will fetch the opcode information, which will be stored into the upper byte of the IR. If the opcode happens to be for an instruction that includes an

address or value, that information will be fetched from memory and stored into the lower byte of the IR.

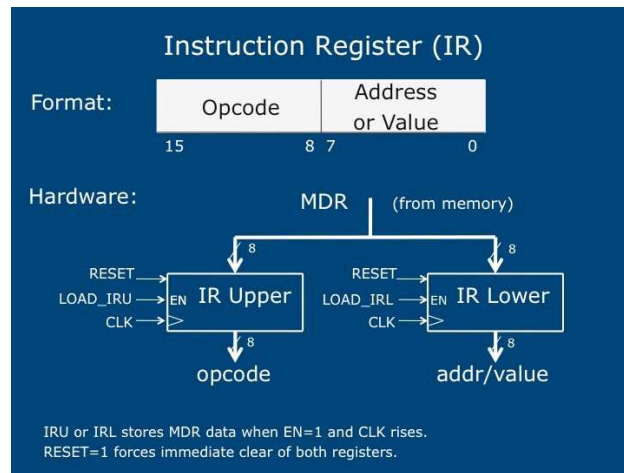


FIG. I.2 The Instruction Register format and hardware

The Program Counter is actually an 8-bit wide sequential device that can be cleared (store a zero), loaded with a new value, or incremented (add 1 to the current value). Since the PC contains the memory address of an instruction, we will use its contents to send to memory as an address.

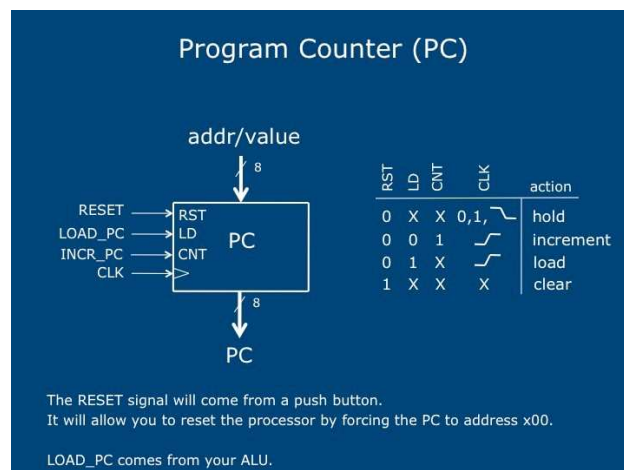


FIG. I.3 The Program Counter state machine

### C. Design strategy

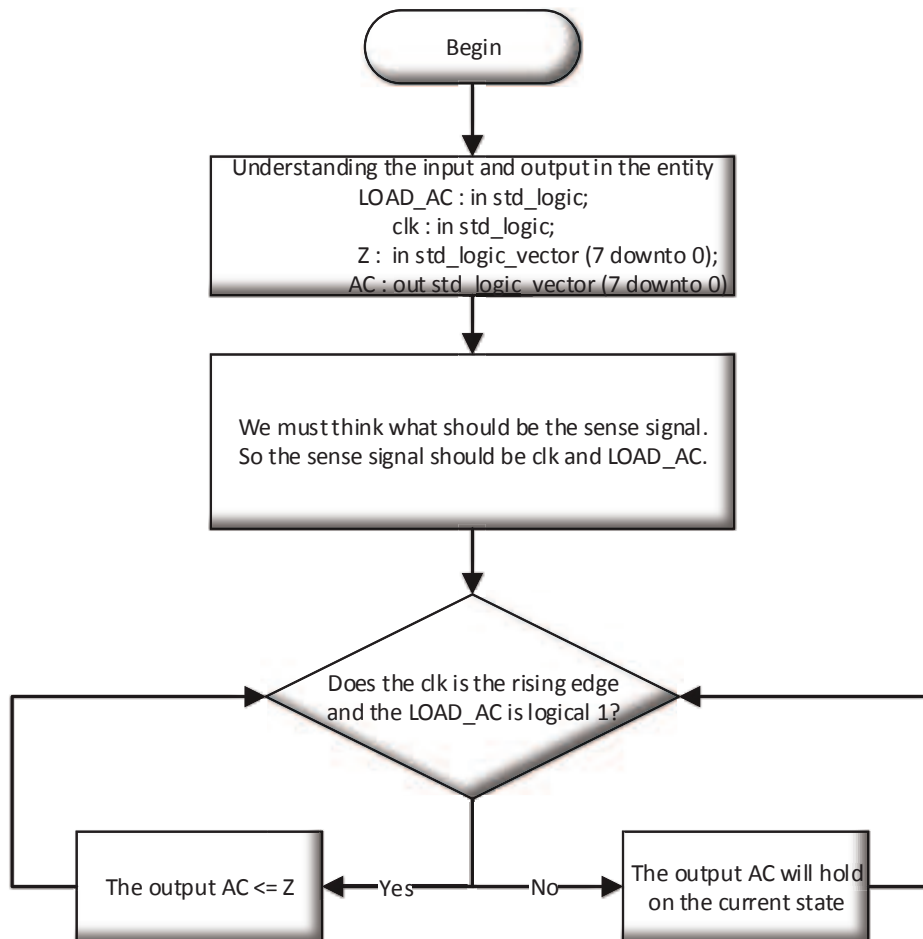


FIG. I.4 The accumulator design strategy

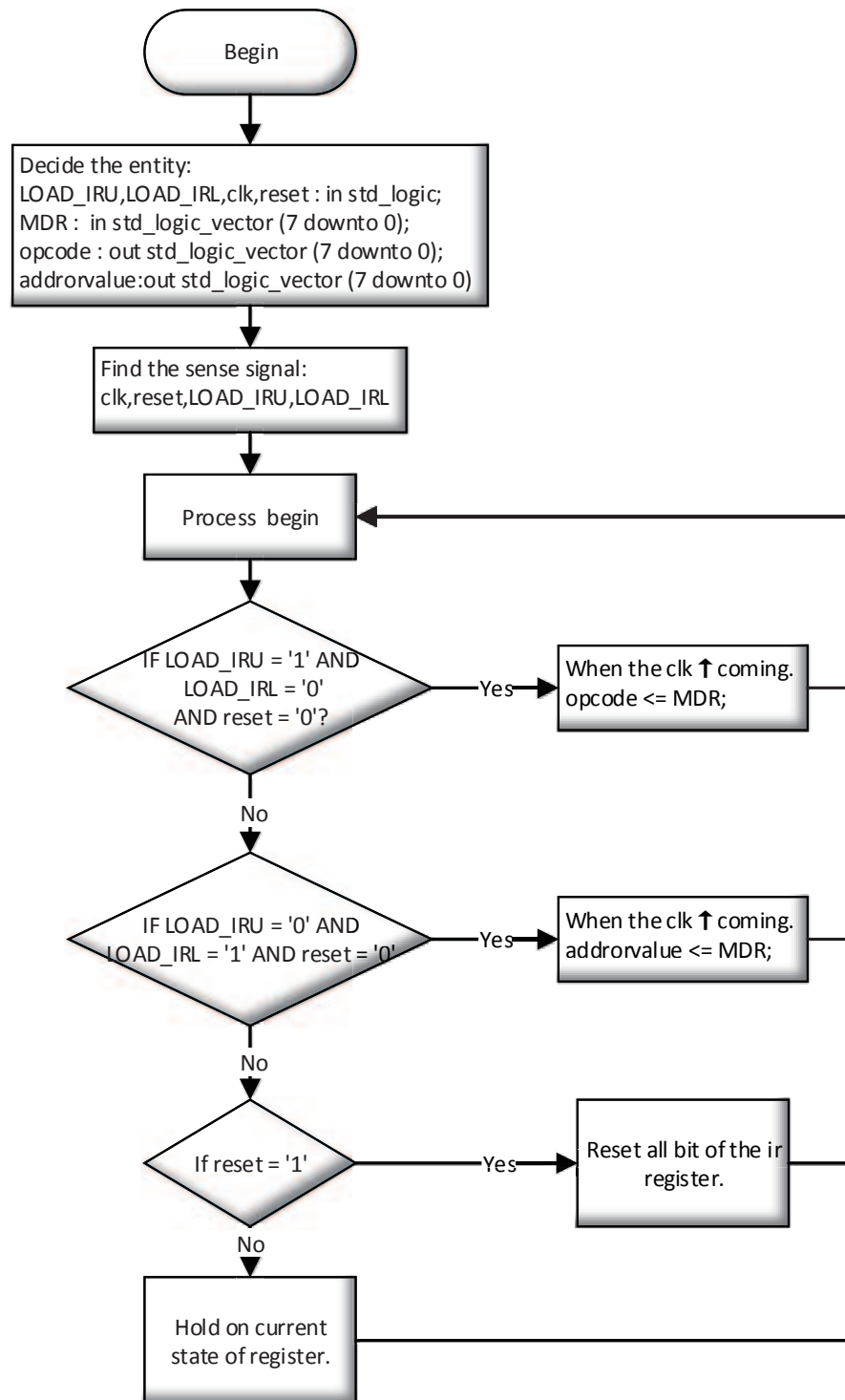


FIG. I.5 The Instruction Register design strategy

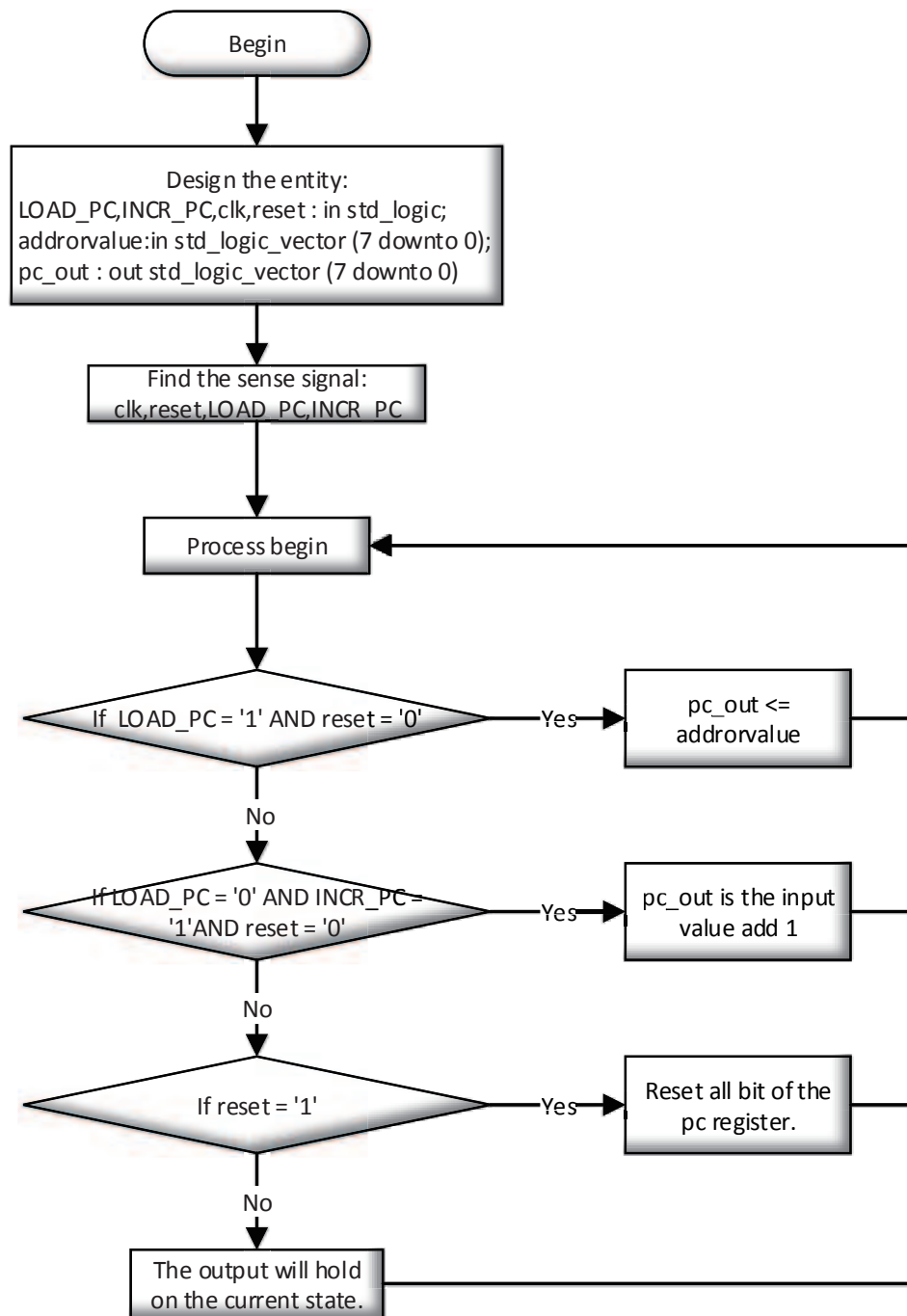


FIG. I.6 The Program Counter design strategy

#### D. Simulation strategy

TABLE I Acculator Demonstration

LOAD_AC	Input signal	clk	Output
low	×	↑	Hold
high	Z	↑	Z
×	×	not↑	Hold

TABLE II Instruction Register Demonstration

reset	LOAD_IRU	LOAD_IRL	MDR[7..0]	clk	seg3, seg2	seg1, seg0
up	×	×	×	×	0	0
down	high	low	Q	↑	Q	Hold
down	low	high	Q	↑	Hold	Q
Other condition: Not change						

TABLE III Program Counter Demonstration

reset	LOAD_PC	INCR_PC	addrorvalue	clk	seg1,seg0
up	×	×	×	×	0
down	high	×	Q	↑	Q
down	low	high	Q	↑	Q+1
Other condition: Not change.					

### E. Demonstration strategy

TABLE IV The Accumulator Set

Input Signal			Output signal
Z[7..0]	LOAD_AC	clk	the HEX1 is upper 4 bit
SW[7..0]	SW8	KEY0	the HEX2 is lower 4 bit

TABLE V Instruction Register Set

Input signal					Output
reset	LOAD_IRU	LOAD_IRL	MDR[7..0]	clk	seg7 display the number of SW[7..0]
KEY1	SW9	SW8	SW[7..0]	KEY0	

TABLE VI Program Counter Set

Input					Output
reset	LOAD_PC	INCR_PC	addrorvalue	clk	pc_out
KEY1	SW8	SW9	SW[7..0]	KEY0	seg1,seg0

## II. LAB DETAILS

### A. Instructor questions in the lab instruction

There is no instructor questions in this lab.

### B. VHDL code

accu.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;

entity accu is
    port(
        LOAD_AC : in std_logic;
        clk : in std_logic;
        Z : in std_logic_vector (7 downto 0);
        AC : out std_logic_vector (7 downto 0)
    );
end entity accu ;

architecture Accumulator of accu is
begin
    -----
    process(LOAD_AC, clk)
    begin
        IF clk'event AND clk = '1' AND LOAD_AC = '1' then
            AC <= Z;--load Z
        END IF;
    end process;
    --other condition will hold on
    -----
end architecture Accumulator ;

```



## IR.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;

entity IR is
    port(
        LOAD_IRU,LOAD_IRL,clk,reset : in std_logic;
        MDR : in std_logic_vector (7 downto 0);--input
        opcode : out std_logic_vector (7 downto 0);--output
        addrorvalue:out std_logic_vector (7 downto 0)--output
    );

    end entity IR ;

    architecture InstructionRegister of IR is
    begin
        -----
        process(clk,reset,LOAD_IRU,LOAD_IRL)
        begin
            -----
            --case1 load opcode
            IF LOAD_IRU = '1' AND LOAD_IRL = '0' AND reset = '0' THEN
                IF clk'event AND clk = '1' THEN
                    opcode <= MDR;
                END IF;
            END IF;

            -----
            --case2 load addr or value
            IF LOAD_IRU = '0' AND LOAD_IRL = '1' AND reset = '0' THEN
                IF clk'event AND clk = '1' THEN
                    addrorvalue <= MDR;
                END IF;
            END IF;

            -----
            --case3 reset
            IF reset = '1' then
                opcode <= "00000000";
                addrorvalue <= "00000000";
            END IF;

            -----
            --other condition hold on
        end process;
        -----
    end architecture InstructionRegister ;
```

## pc.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity pc is
    port(
        LOAD_PC,INCR_PC,clk,reset : in std_logic;
        addrorvalue:in std_logic_vector (7 downto 0);
        pc_out : out std_logic_vector (7 downto 0)
    );
```



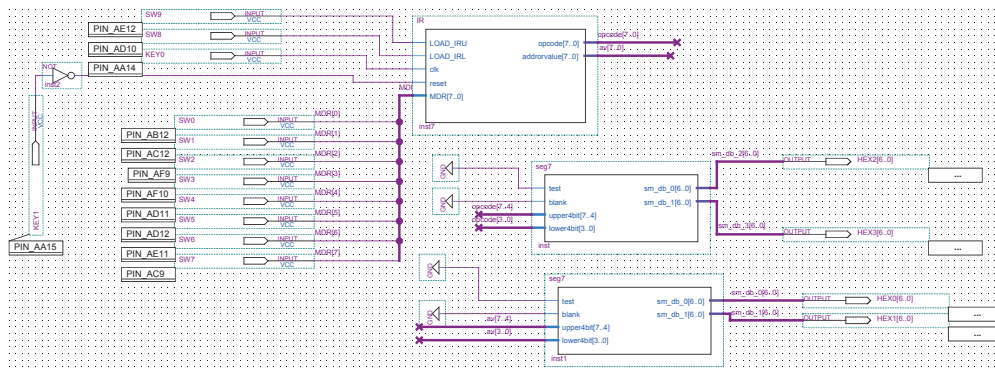


FIG. II.2 IR\_tb Block diagram

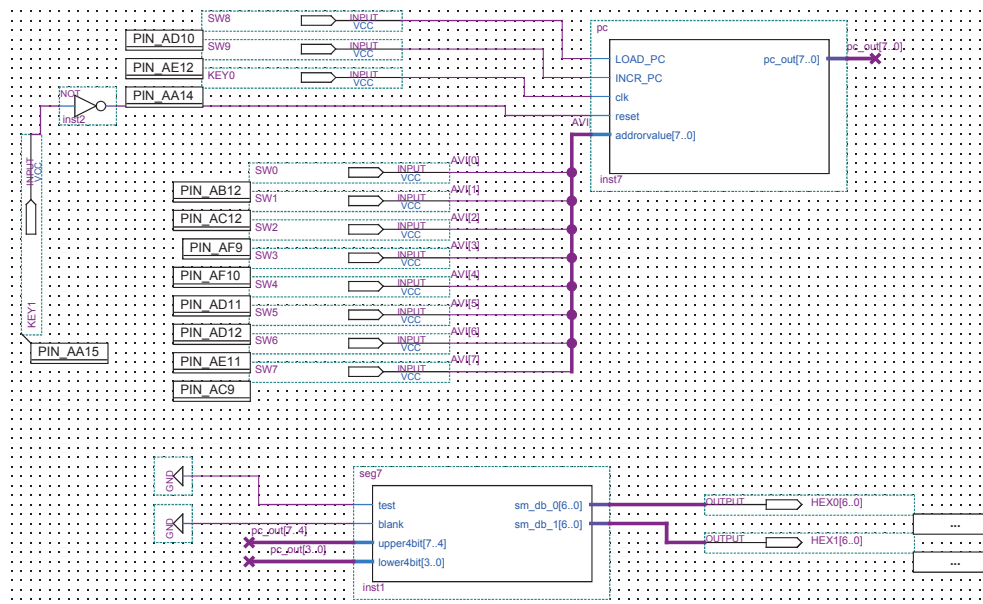


FIG. II.3 pc\_tb Block diagram

#### D. ModelSim force file

accu\_tb.txt:

```
force clk 0 0ns, 1 50ns -r 100ns
force LOAD_AC 1 0ns, 0 800ns -r 1600ns
#when LOAD_AC is 1,output will follow.
force Z 00000001
```

```

run 100ns
force Z 00000010
run 100ns
force Z 00000100
run 100ns
force Z 00001000
run 100ns
force Z 00010000
run 100ns
force Z 00100000
run 100ns
force Z 01000000
run 100ns
force Z 10000000
run 100ns

#when LOAD_AC is 0, output will hold
force Z 00000001
run 100ns
force Z 00000010
run 100ns
force Z 00000100
run 100ns
force Z 00001000
run 100ns
force Z 00010000
run 100ns
force Z 00100000
run 100ns
force Z 01000000
run 100ns
force Z 10000000
run 100ns

```

IR\_tb.txt:

```

force reset 1
run 100ns

#test load opcode
force reset 0

force clk 0 0ns, 1 50ns -r 100ns
force MDR 11111111
force LOAD_IRU 1
force LOAD_JRL 0
run 200ns
force MDR 00000000
run 200ns

# test load addr or value
force MDR 11111111
force LOAD_JRL 1
force LOAD_IRU 0
run 200ns
force MDR 00000000
run 200ns

```

pc\_tb.txt:

```
force clk 0 0ns,1 50ns -r 100ns;#clk set

#test for reset function,all case are 0;
force reset 1
force addrvalue 11111111
force LOAD_PC 1
force INCR_PC 0
run 100 ns
force LOAD_PC 0
force INCR_PC 1
run 100 ns
force LOAD_PC 0
force INCR_PC 0
run 100 ns
force LOAD_PC 1
force INCR_PC 1
run 100 ns

#test for load
force reset 0
force addrvalue 00000000
force LOAD_PC 1
run 200ns;#follow addrvalue when clk at rising edge
force addrvalue 11111111
run 100ns;#follow addrvalue when clk at rising edge

#test for increment
force LOAD_PC 0
force INCR_PC 1
run 400ns; #add 1; shown 0 at begin;
force LOAD_PC 1
force INCR_PC 0
force addrvalue 00000000
run 100ns; #load value 00000000
force INCR_PC 1
force LOAD_PC 0
run 400ns;# add 1; shown 1 at begin
```

## E. Simulation results and detailed explanation

 


FIG. II.4 accu\_tb Wave

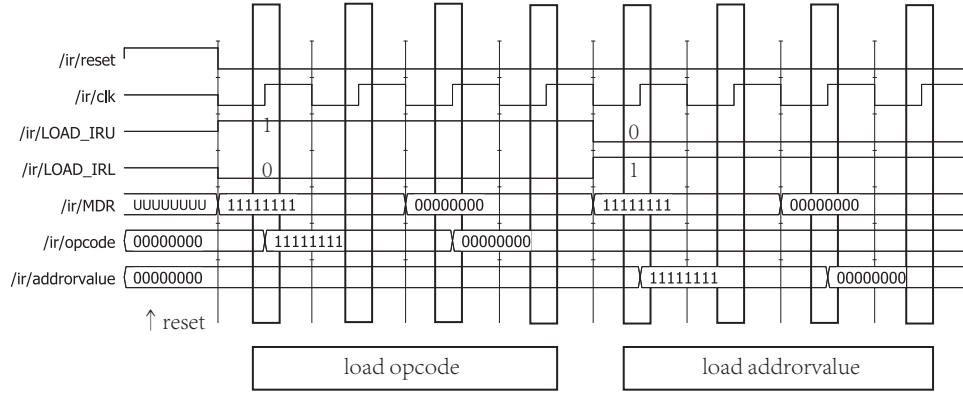


FIG. II.5 IR\_tb Wave

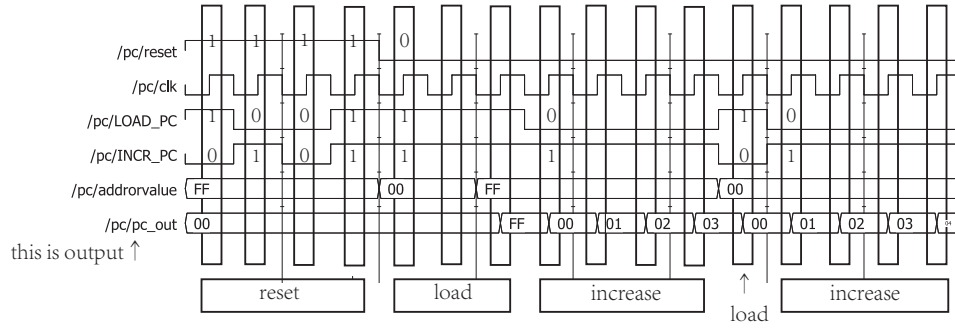


FIG. II.6 pc\_tb Wave

## F. Board demonstration result

TABLE VII Acculator Demonstration

LOAD_AC	Input signal	clk	Output
low	×	↑	Hold
high	Z	↑	Z
×	×	not↑	Hold

TABLE VIII Instruction Register Demonstration

reset	LOAD_IRU	LOAD_IRL	MDR[7..0]	clk	seg3, seg2	seg1, seg0
up	×	×	×	×	0	0
down	high	low	Q	↑	Q	Hold
down	low	high	Q	↑	Hold	Q
Other condition: Not change						

TABLE IX Program Counter Demonstration

reset	LOAD_PC	INCR_PC	addrorvalue	clk	seg1,seg0
up	×	×	×	×	0
down	high	×	Q	↑	Q
down	low	high	Q	↑	Q+1
Other condition: Not change.					

**accu\_tb.sof:**

The logical is the same as Table in the Board demonstration.

**IR\_tb.sof:**

The logical is the same as Table in the Board demonstration.

**pc\_tb.sof:**

The logical is the same as Table in the Board demonstration.

### III. CONCLUSION

The lab is successful.

I realize all function we should achieve. The most difficulty things is the Instructor questions.

I refer to manual and ask classmates that I solved it.